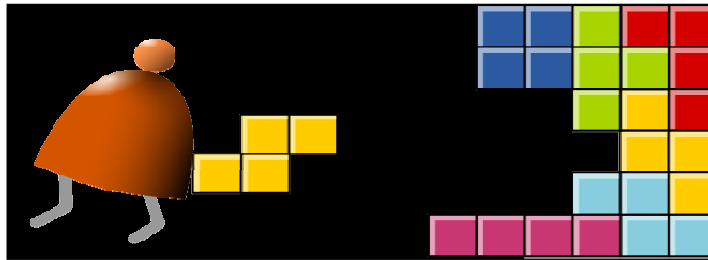


Boolean Arithmetic



Building a Modern Computer From First Principles

www.nand2tetris.org

Counting systems

| quantity | decimal | binary | 3-bit register |
|----------|---------|--------|----------------|
| | 0 | 0 | 000 |
| * | 1 | 1 | 001 |
| ** | 2 | 10 | 010 |
| *** | 3 | 11 | 011 |
| **** | 4 | 100 | 100 |
| ***** | 5 | 101 | 101 |
| ***** | 6 | 110 | 110 |
| ***** | 7 | 111 | 111 |
| ***** | 8 | 1000 | overflow |
| ***** | 9 | 1001 | overflow |
| ***** | 10 | 1010 | overflow |

Rationale

$$(9038)_{ten} = 9 \cdot 10^3 + 0 \cdot 10^2 + 3 \cdot 10^1 + 8 \cdot 10^0 = 9038$$

$$(10011)_{two} = 1 \cdot 2^4 + 0 \cdot 2^3 + 0 \cdot 2^2 + 1 \cdot 2^1 + 1 \cdot 2^0 = 19$$

$$(x_n x_{n-1} \dots x_0)_b = \sum_{i=0}^n x_i \cdot b^i$$

Binary addition

Assuming a 4-bit system:

$$\begin{array}{r} 0\ 0\ 0\ 1 \\ \hline 1\ 0\ 0\ 1 \\ 0\ 1\ 0\ 1 \\ \hline 0\ 1\ 1\ 1\ 0 \end{array} +$$

no overflow

$$\begin{array}{r} 1\ 1\ 1\ 1 \\ \hline 1\ 0\ 1\ 1 \\ 0\ 1\ 1\ 1 \\ \hline 1\ 0\ 0\ 1\ 0 \end{array} +$$

overflow

- Algorithm: exactly the same as in decimal addition
- Overflow (MSB carry) has to be dealt with.

Representing negative numbers (4-bit system)

| | | | |
|---|------|------|----|
| 0 | 0000 | | |
| 1 | 0001 | 1111 | -1 |
| 2 | 0010 | 1110 | -2 |
| 3 | 0011 | 1101 | -3 |
| 4 | 0100 | 1100 | -4 |
| 5 | 0101 | 1011 | -5 |
| 6 | 0110 | 1010 | -6 |
| 7 | 0111 | 1001 | -7 |
| | | 1000 | -8 |

- The codes of all positive numbers begin with a "0"
- The codes of all negative numbers begin with a "1"
- To convert a number:
leave all trailing 0's and first 1 intact,
and flip all the remaining bits

Example: $2 - 5 = 2 + (-5) =$ 0 0 1 0

 + 1 0 1 1

 1 1 0 1 = -3


Building an Adder chip



- Adder: a chip designed to add two integers
- Proposed implementation:
 - Half adder: designed to add 2 bits
 - Full adder: designed to add 3 bits
 - Adder: designed to add two n -bit numbers.

Half adder (designed to add 2 bits)


| a | b | sum | carry |
|---|---|-----|-------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

 

Implementation: based on two gates that you've seen before.

Full adder (designed to add 3 bits)

| a | b | c | sum | carry |
|---|---|---|-----|-------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

 

Implementation: can be based on half-adder gates.


n-bit Adder (designed to add two 16-bit numbers)



| | | | | | |
|-------|---|---|---|---|-----|
| ... | 1 | 0 | 1 | 1 | a |
| | | | | | + |
| ... | 0 | 0 | 1 | 0 | b |
| <hr/> | | | | | |
| ... | 1 | 1 | 0 | 1 | out |

Implementation: array of full-adder gates.

The ALU (of the Hack platform)

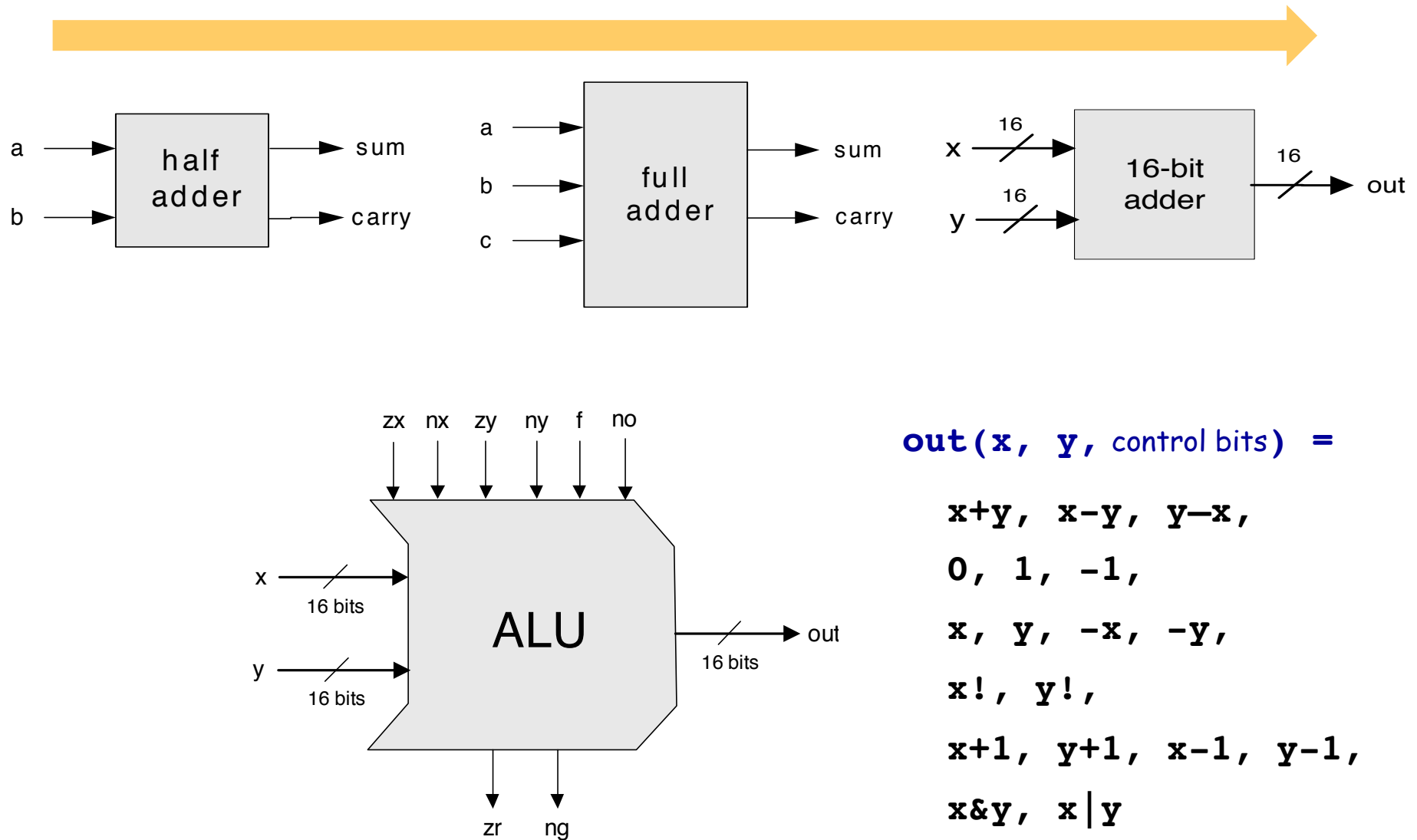


ALU logic (Hack platform)

| These bits instruct how to pre-set the x input | | These bits instruct how to pre-set the y input | | This bit selects between + / And | This bit inst. how to post-set out | Resulting ALU output |
|--|-----------------|--|-----------------|------------------------------------|------------------------------------|----------------------|
| zx | nx | zy | ny | f | no | out= |
| if zx then x=0 | if nx then x=!x | if zy then y=0 | if ny then y=!y | if f then out=x+y else out=x And y | if no then out=!out | f (X, y) = |
| 1 | 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 | 0 | -1 |
| 0 | 0 | 1 | 1 | 0 | 0 | x |
| 1 | | | | | | y |
| 0 | | | | | | !x |
| 1 | | | | | | !y |
| 0 | | | | | | -x |
| 1 | | | | | | -y |
| 0 | 1 | 1 | 1 | 1 | 1 | x+1 |
| 1 | 1 | 0 | 1 | 1 | 1 | y+1 |
| 0 | 0 | 1 | 1 | 1 | 0 | x-1 |
| 1 | 1 | 0 | 0 | 1 | 0 | y-1 |
| 0 | 0 | 0 | 0 | 1 | 0 | x+y |
| 0 | 1 | 0 | 0 | 1 | 1 | x-y |
| 0 | 0 | 0 | 1 | 1 | 1 | y-x |
| 0 | 0 | 0 | 0 | 0 | 0 | x&y |
| 0 | 1 | 0 | 1 | 0 | 1 | x y |

Implementation: build a logic gate architecture that "executes" the control bit "instructions":
if zx==1 then set x to 0 (bit-wise), etc.

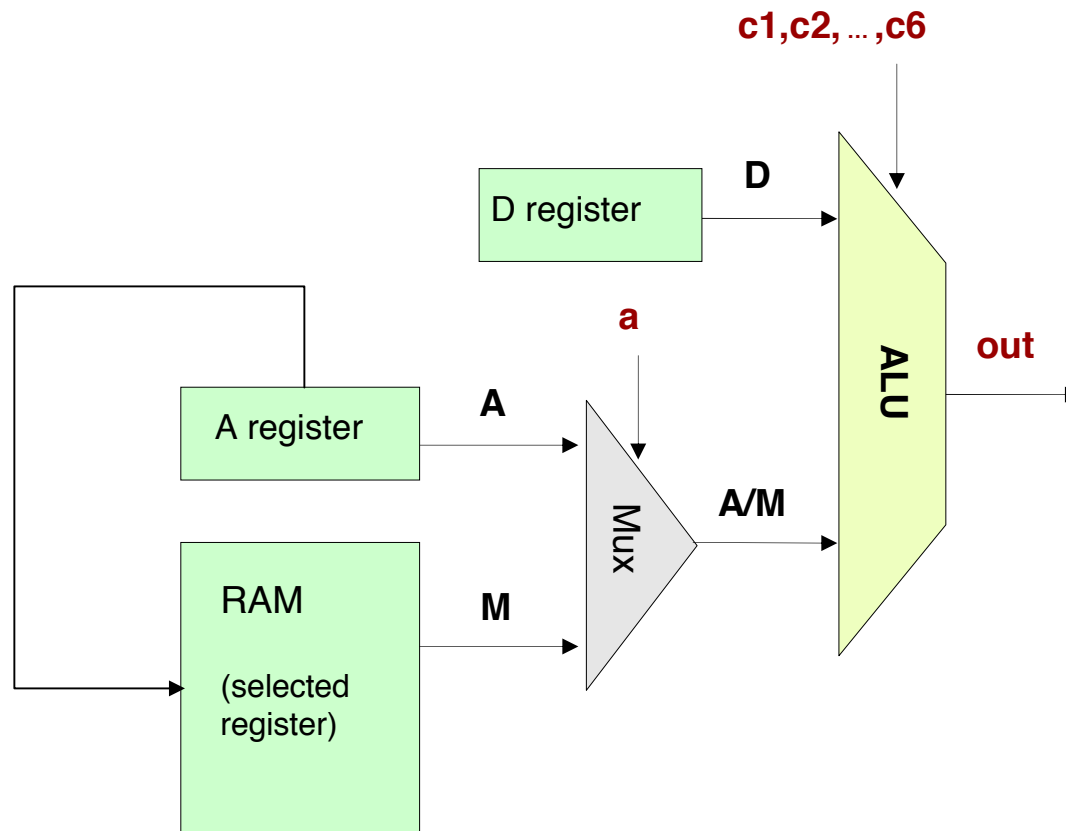The ALU in the CPU context (a sneak preview of the Hack platform)



Perspective

- Combinational logic
- Our adder design is very basic: no parallelism
- It pays to optimize adders
- Our ALU is also very basic: no multiplication, no division
- Where is the seat of more advanced math operations?
a typical hardware/software tradeoff.

Historical end-note: Leibnitz (1646-1716)



- "The binary system may be used in place of the decimal system; express all numbers by unity and by nothing"
- 1679: built a mechanical calculator (+, -, *, /)



- CHALLENGE: "All who are occupied with the reading or writing of scientific literature have assuredly very often felt the want of a common scientific language, and regretted the great loss of time and trouble caused by the multiplicity of languages employed in scientific literature:
- SOLUTION: "*Characteristica Universalis*": a universal, formal, and decidable language of reasoning
- The dream's end: Turing and Gödel in 1930's.

